

Current Electricity



Outline

- Electric current,
- potential difference,
- resistance and resistivity,
- Ohm's law, Ohmic and non-ohmic conductors,
- resistors in series and in parallel,
- electromotive force and circuit,
- electrical energy,
- electrical power and efficiency

Electric Current

The **electric current** is defined as the charge (ΔQ) passing through a given cross-sectional area A of a wire per unit time, that is,

$$I = \frac{\Delta Q}{\Delta t}$$

The unit of current is Coulomb per second, which is called ampere (A).

$$I = \frac{dQ}{dt} \quad \text{differential form}$$

The total charge Q that passes through area A in a time t is $Q = qnAv_d t$

where n = number of charges q per unit volume and v_d = drift velocity of the charges

Electric Current

$$I = \frac{Q}{t} = qnAv_d$$

The **current density** is defined as electric current per unit cross-sectional area. For a uniform current flow, we have,

$$J = \frac{I}{A} = qnv_d$$

The S.I. unit of J is ampere per metre square (Am^{-2}).

Ex 1: A copper wire has a square cross section, 2.0 mm on a side. It carries a current of 10 A. If the density of free electron is $8 \times 10^{28} \text{ m}^{-3}$, calculate the current density in the wire and the drift speed.

$$J = \frac{I}{A} = \frac{10}{4 \times 10^{-6}} \text{ Am}^{-2} = 2.5 \times 10^6 \text{ Am}^{-2}$$

$$v = \frac{J}{nq} = \frac{2.5 \times 10^6}{8 \times 10^{28} \times 1.6 \times 10^{-19}} \text{ m/s} = 1.953 \times 10^{-4} \text{ m/s}$$



Ohm's Law

Ohm's law states that under constant physical conditions, the current in a conducting wire is proportional to the potential difference V applied to its ends.

$$I \propto V \quad \text{which implies} \quad I = \frac{V}{R}$$

It is found experimentally that the resistance R of a wire is proportional to the length of the wire and inversely proportional to the cross-sectional area A , that is

$$R \propto \frac{L}{A} \quad \text{which implies} \quad R = \rho \frac{L}{A}$$

where ρ is the constant of proportionality which is known as the **resistivity** of the material. The resistivity ρ depends only on the material and the temperature. The unit of resistivity ρ is ohm-metre (Ωm).

Conductivity, σ , is the reciprocal of the resistivity, that is

$$\sigma = \frac{1}{\rho} \quad (\Omega\text{m})^{-1}$$



Ohmic and Non Ohmic Conductors

Ohmic conductors are conductors that obey Ohm's law.

–the characteristic or I – V graph is a straight line passing through the origin.

For example, copper and tungsten obey Ohm's law.

Non-ohmic conductors are those which do not obey Ohm's law.


For example, junction diode, neon gas, diode valve, dilute H_2SO_4 (platinum electrodes) do not obey Ohm's law.

A non-ohmic characteristic or I – V graph may have a curve instead of a straight line; or it may not pass through the origin.



Resistors in series and parallel

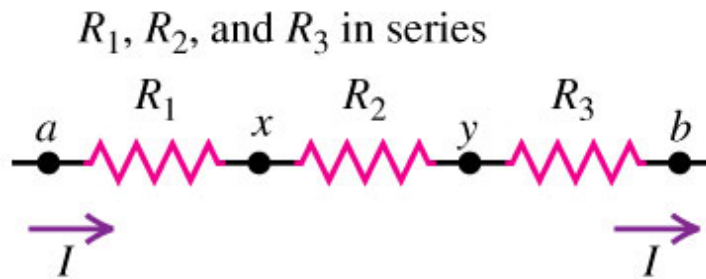- Resistors are in **series** if they are connected one after the other so the current is the same in all of them.
- The **equivalent resistance** of a series combination is the *sum* of the individual resistances: $R_{eq} = R_1 + R_2 + R_3 + \dots$



Series Resistors
have resistance
LARGER than the
largest value
present.


- The same current flows through all resistors in series
- Total potential difference = sum of individual potential differences
 $V = V_1 + V_2 + V_3$
- Individual potential differences is directly proportional to individual resistances
 $V_1 = IR_1, V_2 = IR_2 \text{ and } V_3 = IR_3$



Resistors in series and parallel

- Resistors are in **parallel** if they are connected so that the potential difference must be the same across all of them.
- The *equivalent resistance* of a parallel combination is given by
$$1/R_{eq} = 1/R_1 + 1/R_2 + 1/R_3 + \dots$$

R_1, R_2 , and R_3 in parallel

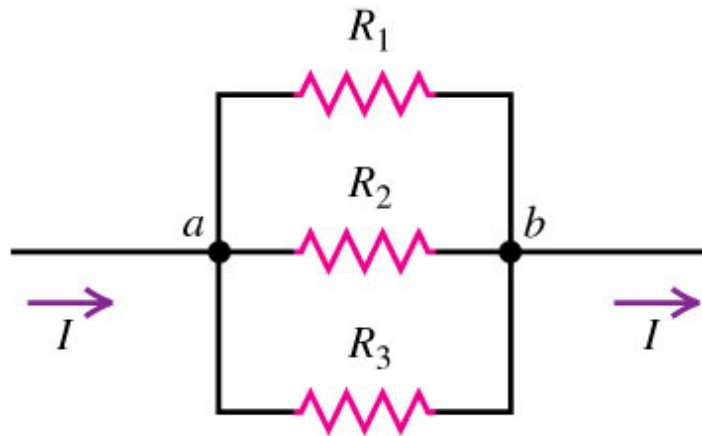

Parallel Resistors
have resistance
SMALLER than the
smallest value
present.

- Total current, I is equal to sum of individual currents flowing through the resistors in parallel; $I = I_1 + I_2 + I_3$
- The potential difference across each resistor is the same and is equal to the full voltage V .
- Individual current is inversely proportional to individual resistances


$$V = I_1 R_1, V = I_2 R_2 \text{ and } V = I_3 R_3$$




Series and parallel combinations

- Resistors can be connected in combinations of series and parallel

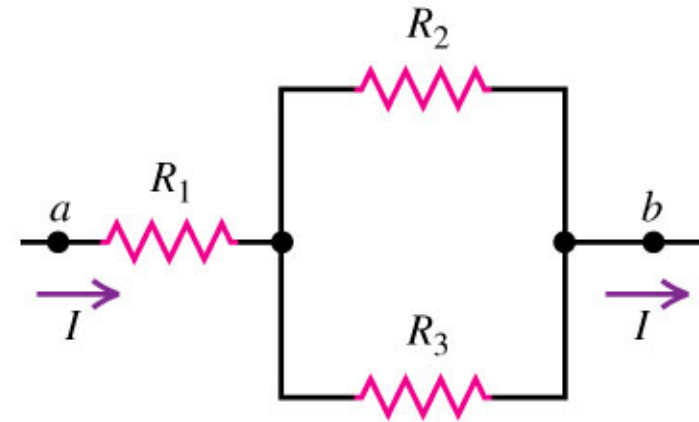(c) R_1 in series with parallel combination of R_2 and R_3



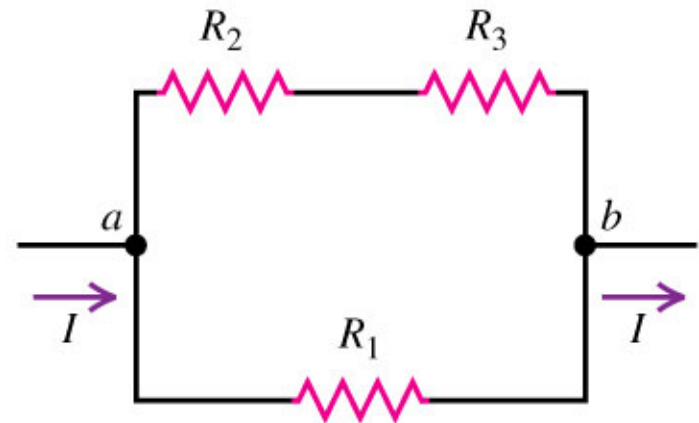(d) R_1 in parallel with series combination of R_2 and R_3




Electromotive force and Circuit

- The **electromotive force** or e.m.f. (E) is the potential difference across the terminals of a battery (or any other generator) on open circuit, that is, when no current is flowing.
- The e.m.f. of a battery depends on the nature of the chemicals used and not on its size.
- However, the internal resistance, r , of the battery depends on the size of the battery.



Electromotive force and Circuit

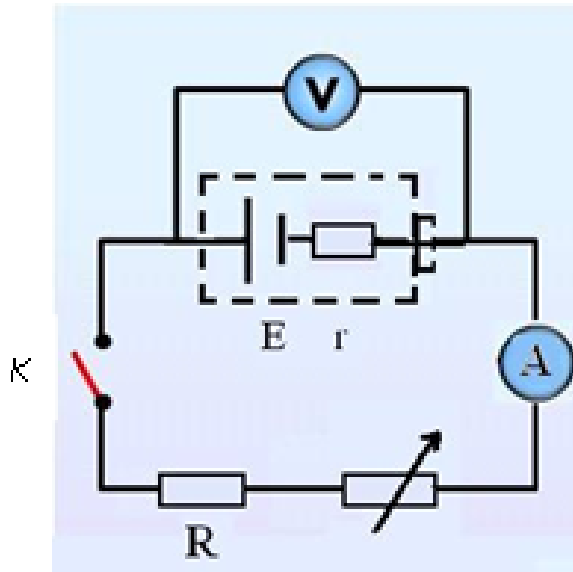

$$I = \frac{E}{R + r}$$

Terminal p.d. $V = IR = \frac{ER}{R + r}$,

Example 2: A battery of e.m.f. 4V and internal resistance $2\ \Omega$ is joined to a resistor of $8\ \Omega$. Calculate the terminal p.d.

$$I = \frac{E}{R + r} = \frac{4}{8 + 2} \text{ A} = 0.4 \text{ A}$$

$$V = IR = 0.4 \times 8 \text{ V} = 3.2 \text{ V}$$



Electrical Power and Efficiency

The electrical work (W) required to transfer a charge q through a potential difference V is given by

$$W = qV$$

Electrical Power $P = \frac{\text{Electrical Work}}{\text{Time}} = \frac{qV}{t} = VI$

The unit of power is watt ($1\text{ W} = 1\text{ J/s}$).

We can also define the e.m.f. E of a battery or any other generator as the total energy per coulomb it delivers round a circuit joined to it.

Total electrical power generated is

$$P = \frac{W}{t} = EI$$



Electrical Power and Efficiency

Efficiency, η , of a circuit is the ratio of the power output to the power generated:

$$\eta = \frac{\text{Power output}}{\text{Power generated}}$$


$$\eta = \frac{P_{out}}{P_{gen}} = \frac{IV}{IE} = \frac{V}{E}$$

$$\eta = \frac{R}{R + r} \quad \text{How come?}$$









Equivalent resistance

- Example 3

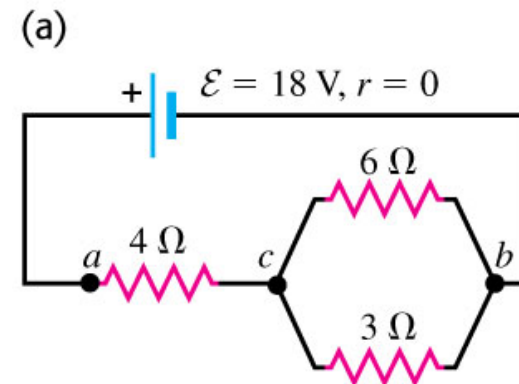


Equivalent resistance

- Example 3

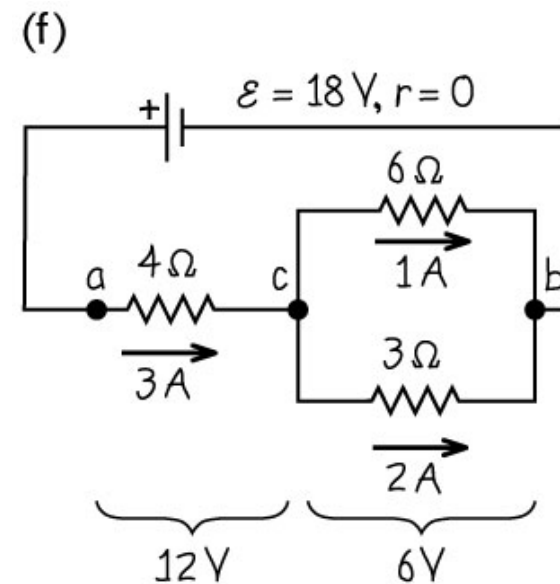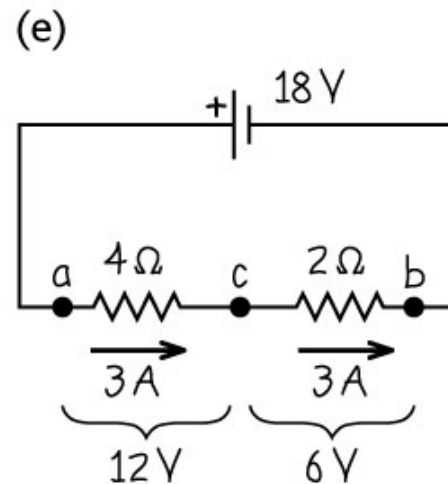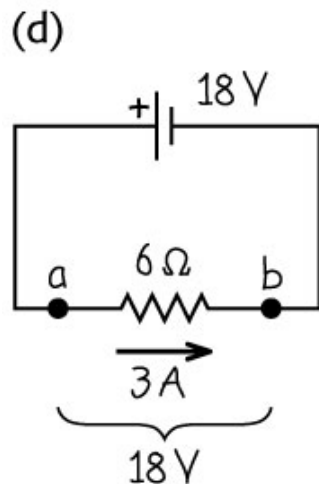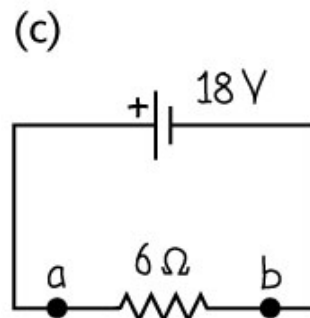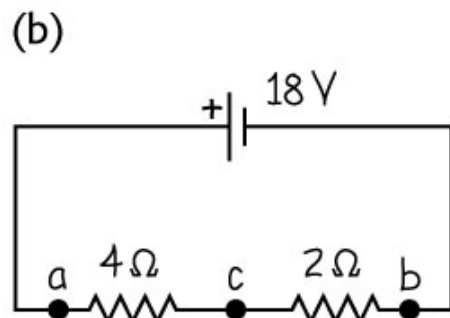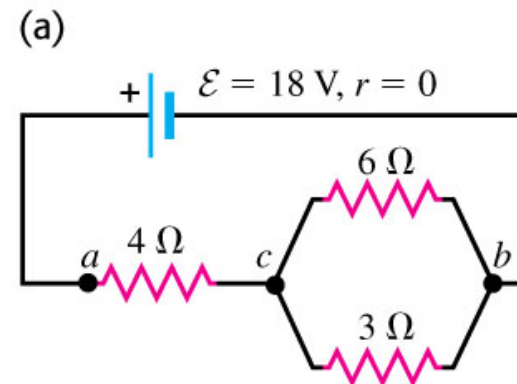

Series versus parallel combinations

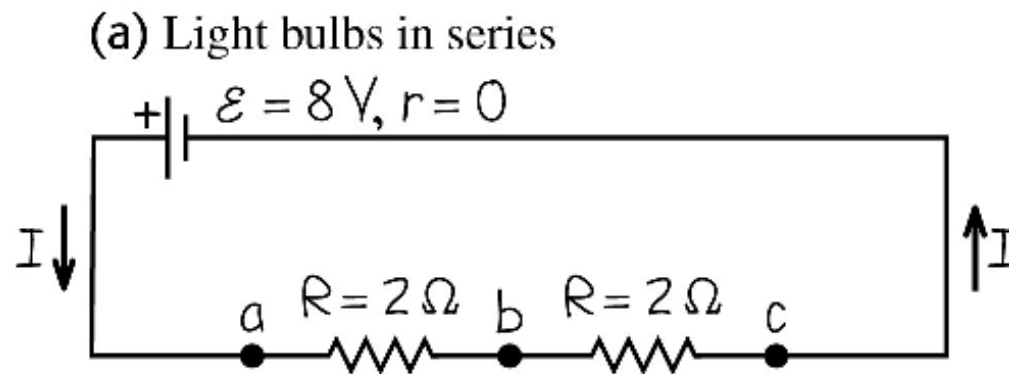
- Ex 4: Current through each R & Power dissipated?



- $R_{\text{equivalent}} = 2 + 2 = 4\text{ Ohms}$
- $I = 8\text{ V} / 4\ \Omega = 2\text{ A}$
- Power = $i^2 R = 16\text{ Watts total (8 Watts for each bulb)}$

Series versus parallel combinations

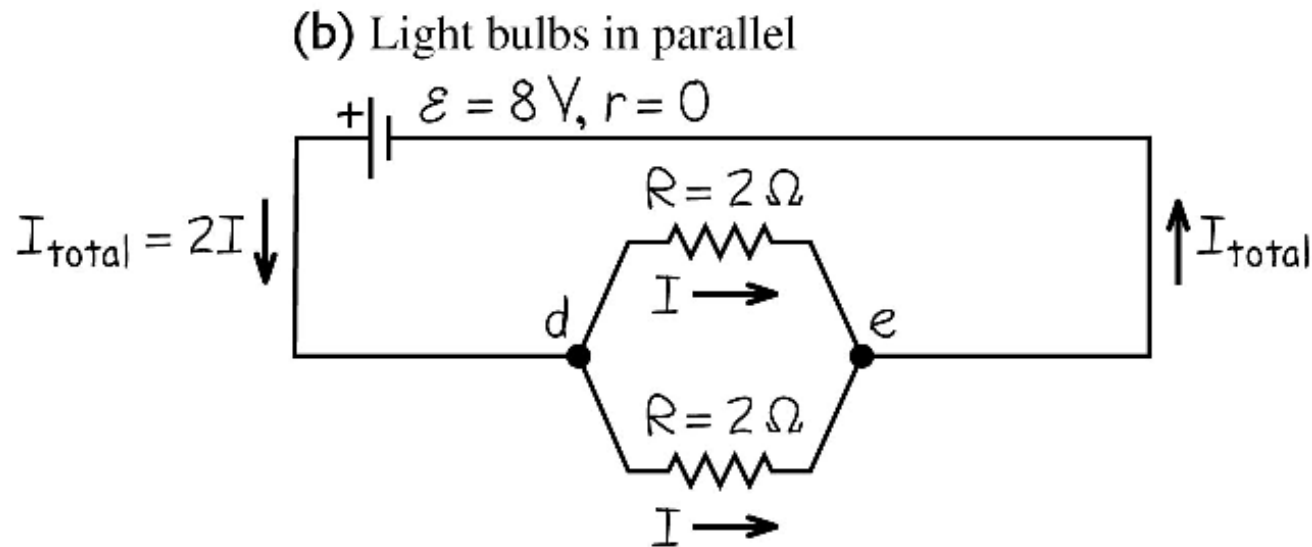- Ex 5: Current through each R & Power dissipated?




- $R_{\text{equivalent}} = (\frac{1}{2} + \frac{1}{2})^{-1} = 1\ \text{Ohm}$
- $I = 8\text{ V} / 1\ \Omega = 8\ \text{A}$
- Power = $i^2 R = 64\ \text{Watts total}$ (32 Watts for each bulb)

Adding Capacitors to DC circuits!

- RC circuits include

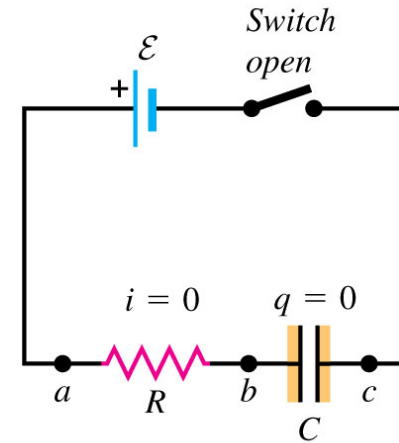- Batteries (Voltage sources!)
- Resistors
- Capacitors
- ... and switches!




- RC circuits will involve **TIMING** considerations
 - Time to *fill up* a capacitor with charge
 - Time to *drain* a capacitor that is already charged




Charging a capacitor

- Start with uncharged capacitor! What happens??


(a) Capacitor initially uncharged

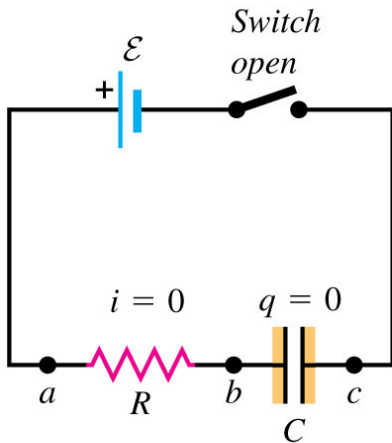

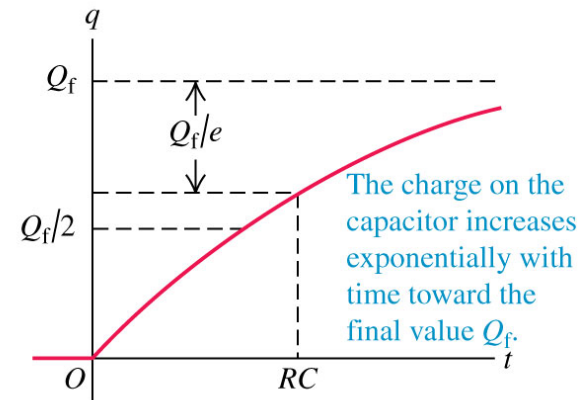(b) Graph of capacitor charge versus time for a charging capacitor




(b) Charging the capacitor

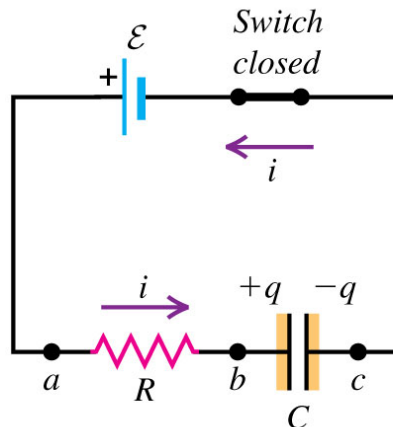


When the switch is closed, the charge on the capacitor increases over time while the current decreases.

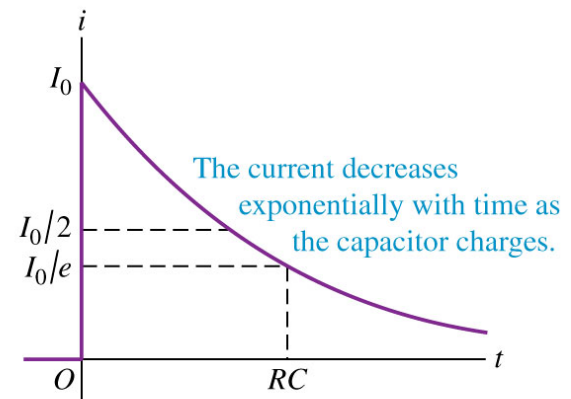(a) Graph of current versus time for a charging capacitor



Adding Capacitors to DC circuits!

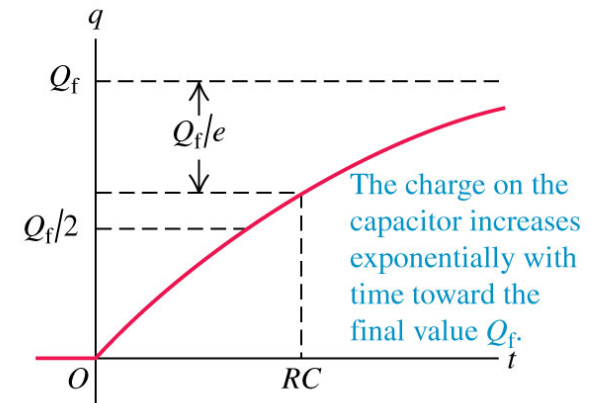
- In charging RC circuits the *time constant* is τ
- τ *increases with R*
 - Larger resistors decrease current
 - Less charge/time arrives at capacitor
 - It takes longer to fill up capacitor
- τ *increases with C*
 - Larger capacitors have more capacity!
 - They take longer to fill up!




Charging a capacitor

- The *time constant* is $\tau = RC$.
- In ONE time constant:
 - Current drops to $1/e$ of initial value (about 36%)
 - Charge on capacitor plates rises to $\sim 64\%$ of maximum value


(a) Capacitor initially uncharged

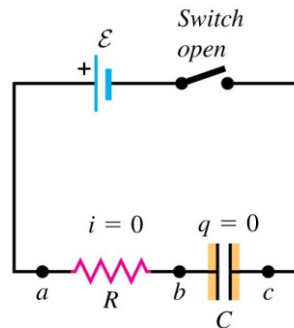


(b) Charging the capacitor

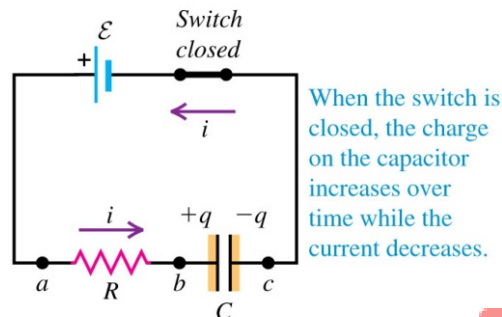

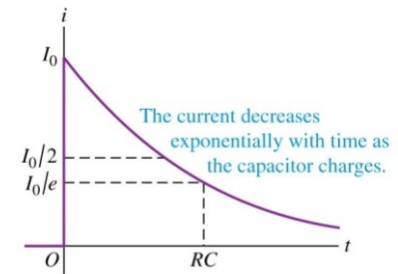(a) Graph of current versus time for a charging capacitor



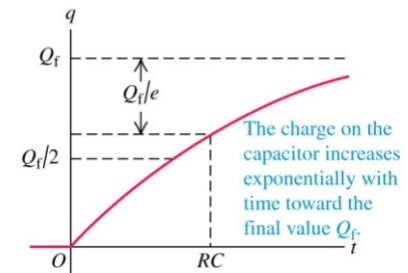
(b) Graph of capacitor charge versus time for a charging capacitor



Charging a Capacitor

- $V_{ab} = iR$
- $C = q/V_{bc}$ so $V_{bc} = q/C$
- $E - iR - q/C = 0$

(b) Charging the capacitor

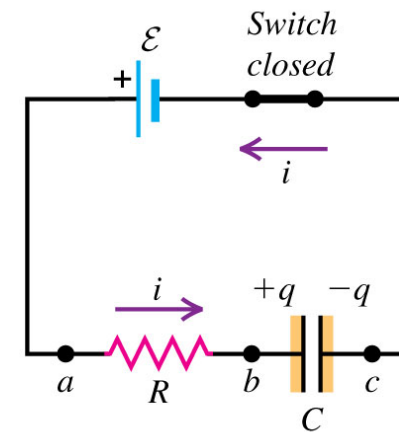


When the switch is closed, the charge on the capacitor increases over time while the current decreases.

- Current is a function of time
- $i = dq/dt$
- $E - (dq/dt)R - q(t)/C = 0$
- *A differential equation involving charge q*

Charging a Capacitor

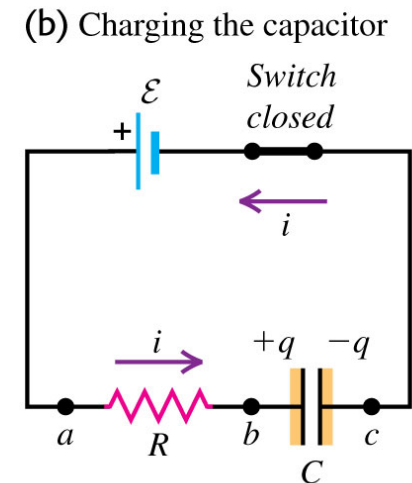
- $E - (dq/dt)R - q/C = 0$
- *Boundary conditions* relate q and t at key times:
 - $q(t)$ on capacitor = 0 @ $t=0$
 - $q = Q_{\max}$, $i(t) = 0$ @ $t = \infty$ (when capacitor is full)



Charging a Capacitor

- $E - iR - q/C = 0$
- General Solution
- $q(t) = Q_{\max} (1 - e^{-t/RC})$
- Check?

(b) Charging the capacitor

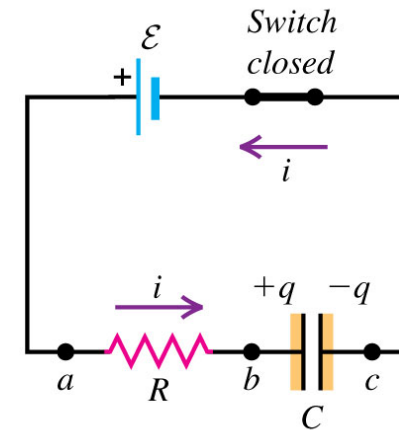

When the switch is closed, the charge on the capacitor increases over time while the current decreases.

- $q(t)$ on capacitor = 0 @ $t=0$
- $i(t) = dq/dt = Q_{\max}/RC e^{-t/RC}$
- $i(0)$ is maximum current, $Q_{\max}/RC = E/R = I_0$
- $i(t) = 0$ when capacitor is full, @ $t = \infty$

Charging a capacitor

- $10\text{ M}\Omega$ resistor connected in series with $1.0\text{ }\mu\text{F}$ uncharged capacitor and a battery with emf of 12.0 V .
 - What is time constant?
 - What fraction of final charge is on capacitor after 46 seconds?
 - What fraction of initial current I_0 is flowing then?



Charging a capacitor


- 10 M Ω resistor connected in series with 1.0 μ F uncharged capacitor and a battery with emf of 12.0 V.
 - What is time constant?
 - What fraction of final charge is on capacitor after 46 seconds?
 - What fraction of initial current I_0 is flowing then?
- $\tau = RC = 10$ seconds
- $Q(t) = Q_{\max} (1 - e^{-t/RC})$ so $Q(46 \text{ seconds})/Q_{\max} = 99\%$
- $I(t) = I_0 e^{-t/RC}$ so $I(46 \text{ seconds})/I_0 = 1\%$




Discharging a capacitor

- Disconnect Battery – let Capacitor “drain”


(a) Capacitor initially charged

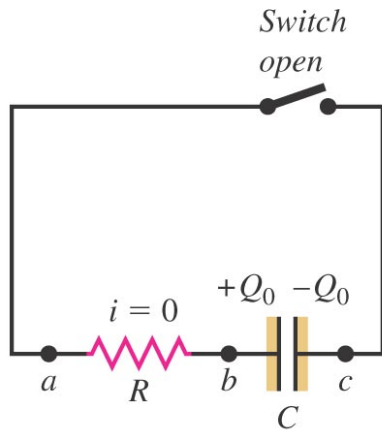


(b) Discharging the capacitor

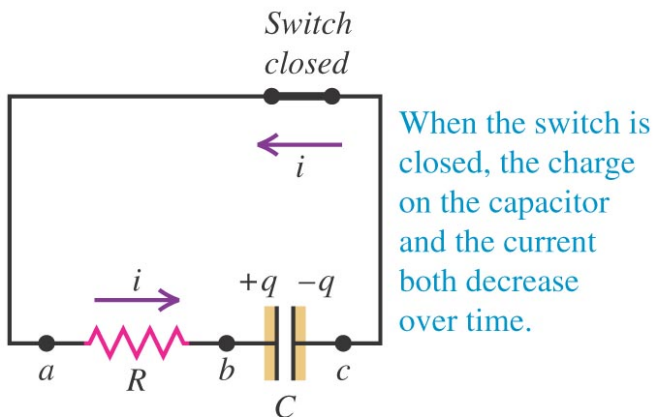

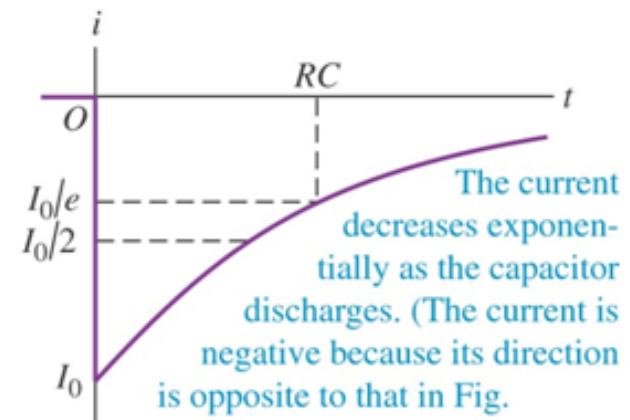(a) Graph of current versus time for a discharging capacitor



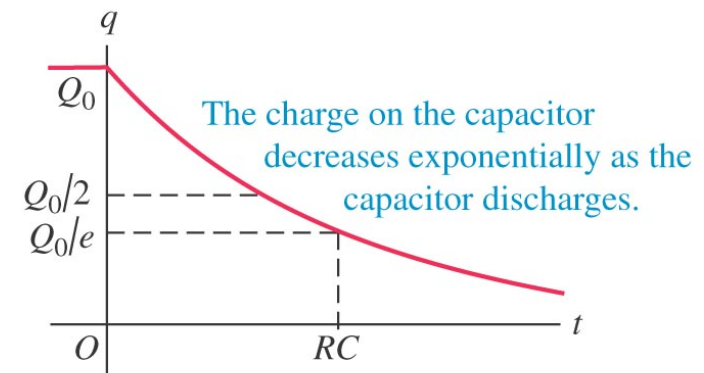
(b) Graph of capacitor charge versus time for a discharging capacitor



Adding Capacitors to DC circuits!

- In discharging RC circuits the *time constant* is still τ
- τ *increases* with R
 - Larger resistors decrease current
 - Less charge/time *leaves* capacitor
 - It takes longer to *drain* capacitor
- τ *increases* with C
 - Larger capacitors have more capac
 - They take longer to *drain*!

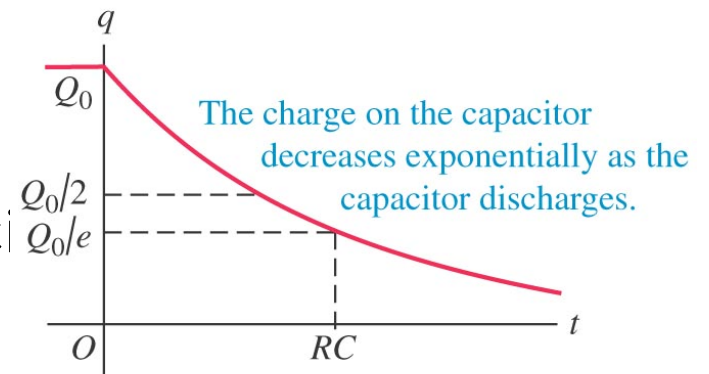
(b) Graph of capacitor charge versus time for a discharging capacitor




Discharging a capacitor

- Time constant is still RC !
- In one time constant:
 - Charge on plates DROPS by 64%
 - Current through resistor DROPS by 64% (“negative”)


(a) Capacitor initially charged

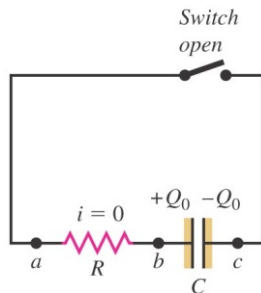


(b) Discharging the capacitor

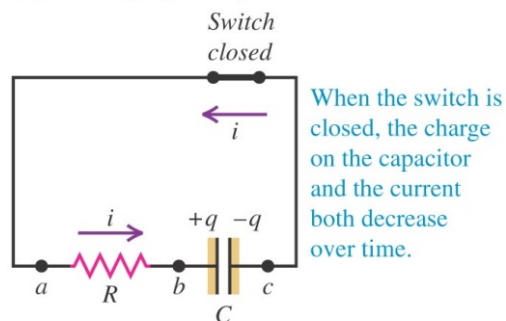

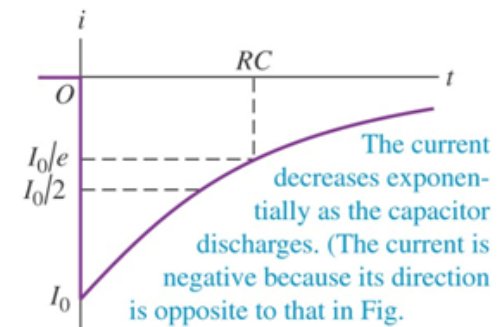(a) Graph of current versus time for a discharging capacitor



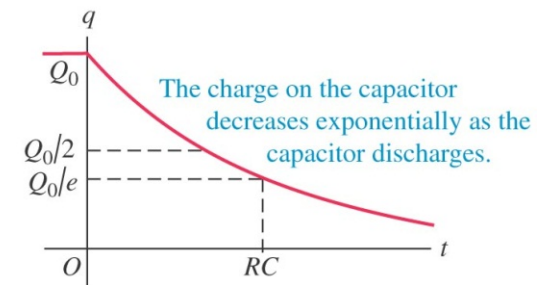(b) Graph of capacitor charge versus time for a discharging capacitor




Charging a Capacitor

- $V_{ab} = iR$
- $V_{bc} = q/C$
- $iR + q/C = 0$


- Another differential equation involving charge
- $i = dq/dt$
- $(dq/dt)R + q(t)/C = 0$

(b) Discharging the capacitor

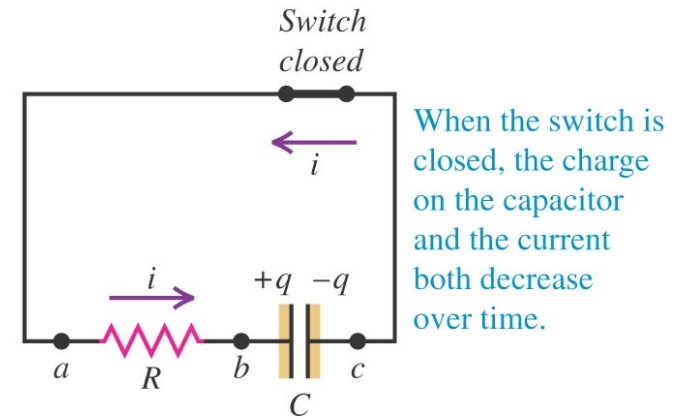

Charging a Capacitor

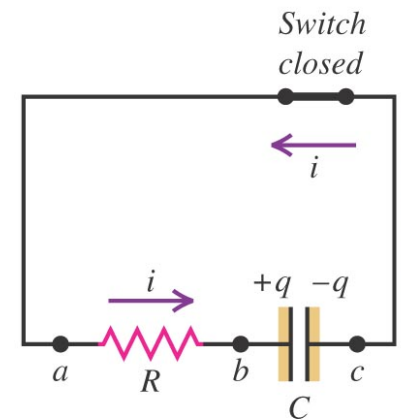- $iR + q/C = 0$
- $(dq/dt)R + q(t)/C = 0$
- Boundary conditions:
 - $q(t)$ on capacitor = $Q_{\max}$ @ $t=0$
 - $q=0, i(t)=0$ @ $t=\infty$
when capacitor is *empty*



Charging a Capacitor

- $iR + q/C = 0$

- General Solution

- $q(t) = Q_{\max} e^{-t/RC}$


- $i = dq/dt = I_0 e^{-t/RC}$

- Check

- $q(t)$ on capacitor = $Q_{\max}$ @ $t=0$

- $q=0, i(t)=0$ when capacitor is empty,
@ $t = \infty$

(b) Discharging the capacitor

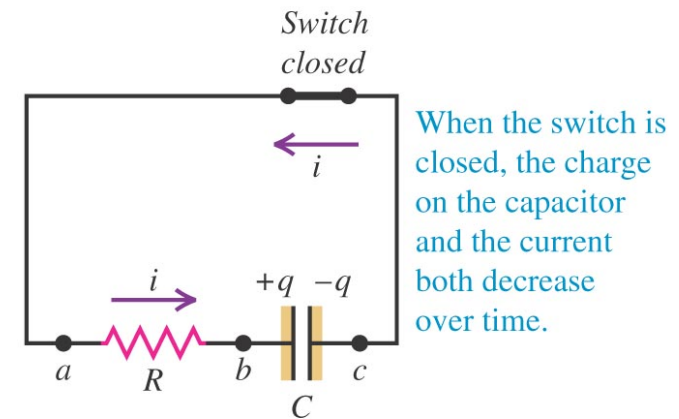

Discharging a capacitor

- Same circuit as before; $10\text{ M}\Omega$ resistor connected in series with $1.0\text{ }\mu\text{F}$ capacitor; battery with emf of 12.0 V is disconnected.
- Assume at $t = 0$, $Q(0) = 5.0\text{ }\mu\text{C}$.
- When will charge = $0.50\text{ }\mu\text{C}$?
- What is current then?



Discharging a capacitor

- Same circuit as before; $10\text{ M}\Omega$ resistor connected in series with $1.0\text{ }\mu\text{F}$ capacitor; battery with emf of 12.0 V is disconnected.
- Assume at $t = 0$, $Q(0) = 5.0\text{ }\mu\text{C}$.
- When will charge = $0.50\text{ }\mu\text{C}$?
- What is current then?
- $\tau = RC = 10\text{ seconds}$ (still!)
- $Q(t) = Q_{\text{max}} e^{-t/RC}$ so $Q(t) = 1/10^{\text{th}} Q_{\text{max}} \Rightarrow$
 $t = RC \ln(Q/Q_{\text{max}}) = 23\text{ seconds}$ (2.3τ)
- $I(t) = -Q_0/RC (e^{-t/RC})$ so $I(2.3\tau) = -5.0 \times 10^{-8}\text{ Amps}$



Assignment (Submission deadline – 08/04/2015; 2pm)

- 13.1. Figure 13.19 shows a battery of 12 V and negligible internal resistance connected to three resistors. Calculate the p.d. V across the $6\ \Omega$ resistor and the current passing through the $8\ \Omega$ resistor.

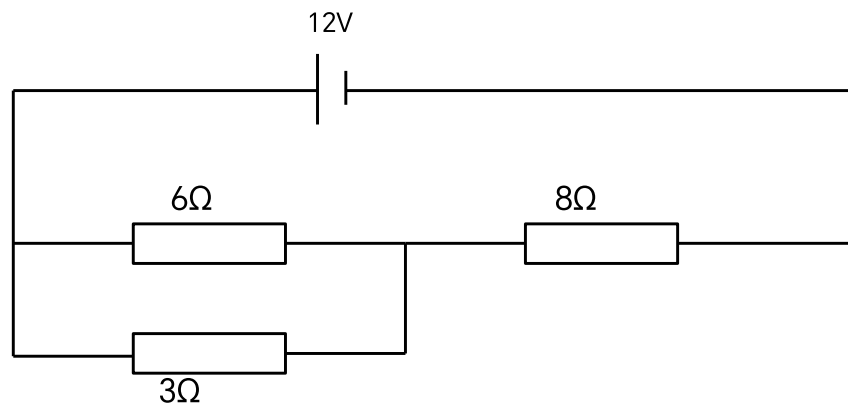


Figure 13.19: SAQ 13.1



Assignment

- **13.2.** A battery of e.m.f. 8 V and internal resistance r is connected to a $10\ \Omega$ resistor. Given that the terminal p.d. across the resistor is 5 V, calculate the value of the internal resistance of the battery.
- **13.3.** A battery X of e.m.f. of 6 V and internal resistance $2\ \Omega$ is connected in series with a battery Y of e.m.f. 4 V and internal resistance $8\ \Omega$ so that the two e.m.f.s act to oppose each other, calculate the terminal p.d. of X and Y .
- **13.4.** A light bulb has a resistance of $60\ \Omega$ when lit. How much current will flow through it when it is connected across 120 V, its normal operating voltage?
- **13.5.** A dry cell has an e.m.f. of 1.50 V. Its terminal potential drops to zero when a current of 10 A passes through it. What is its internal resistance?
- **13.6.** A metal rod is 2 m long and 8 mm in diameter. Calculate its resistivity if the resistance of the rod is $7 \times 10^{-8}\ \Omega$.
- **13.7.** The constant resistance of a resistor is $30.0\ \Omega$, independent of the temperature. The resistor is made up of an aluminum resistor with resistance R_1 at 0°C in series with a carbon resistor with resistance R_2 at 0°C . Evaluate R_1 and R_2 , given that the temperature coefficient for aluminum and carbon are $3.9 \times 10^{-3}^\circ\text{C}^{-1}$ and $-0.50 \times 10^{-3}^\circ\text{C}^{-1}$ respectively.

Assignment

- 13.8. State Ohm's law and differentiate between Ohmic and Non-Ohmic conductors.
- 13.9. A wire that has a resistance of $5.0\ \Omega$ is made into a new wire three times as long as the original. What is the new resistance?
- 13.10. How many electrons per second pass through a section of a conductor carrying a current of 0.70 A ?
- 13.11. Calculate the resistance that will be connected in series with a cell of 1.54 V , $0.10\ \Omega$, given that the terminal p.d. is 1.40 V .
- 13.12. A generator supplies a current of 10 A to charge a storage battery which has an open-circuit voltage of 5.6 V . If the voltmeter connected across the generator reads 6.7 V , what is the internal resistance of the generator?
- 13.13. Calculate the resistance of a 110 m long and 1.0 mm diameter aluminum wire of resistivity $2.8 \times 10^{-8}\ \Omega\text{m}$.



Assignment

- 13.14. Three 5 ohms resistors connected in parallel have a potential difference of 60V applied across the combination. The current in each resistor is A. 4A B. 36A C. 12A D. 24A
- 13.15. How much current does a 60 W light bulb draw when connected to its proper voltage, 240 V?
- 13.16. Calculate the current drawn from a heater having 1600 W at 240 V.
- 13.17. Calculate the resistance of a 60 W/120 V bulb.
- 13.18. Sparks of artificial 10.0 MV lightning had energy output of 0.125 MWs. How many coulombs of charge flowed?
- 13.19. 90 C charge is transferred in one minute when a current I flows through a conductor whose terminals are connected across a potential difference of 100 V. Calculate the value of I and the power expended in heating the conductor if all the electrical energy is converted into heat.

